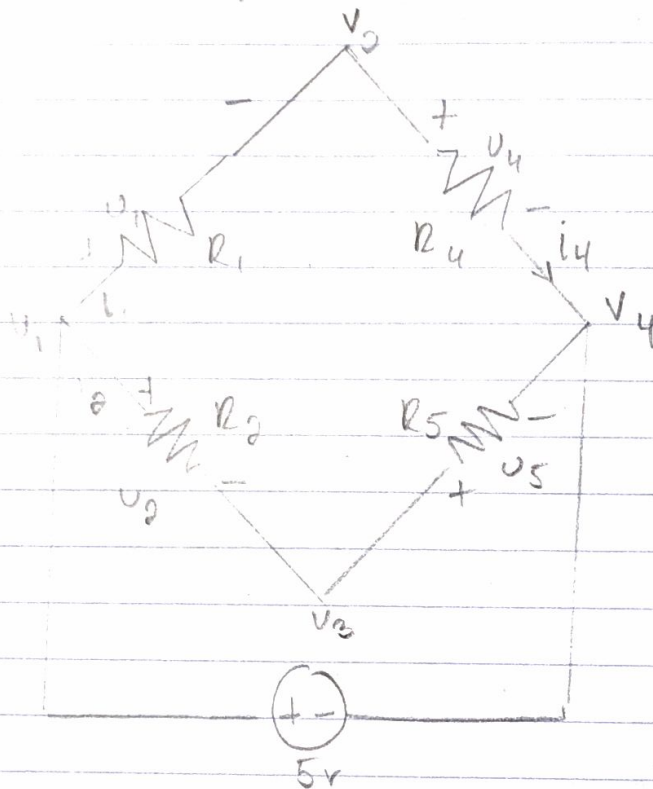


EE 16A Homework # 8

3 Wheatstone Bridge

3A



2 voltage dividers

$$V_4 = \frac{R_1}{R_1 + R_4} (V_1 - V_4)$$

$$V_5 = \frac{R_5}{R_2 + R_5} (V_1 - V_4)$$

A Thevenin voltage is the difference between the two voltages $V_4 - V_5 = (V_1 - V_4) \cdot \frac{R_1(R_2 + R_5) + R_2(R_1 + R_4)}{(R_1 + R_4)(R_2 + R_5)}$

C $R_{th} = (R_1 \parallel R_4) + (R_2 \parallel R_5)$


$$= \frac{R_1 + R_4}{R_1 R_4} + \frac{R_2 + R_5}{R_2 R_5} = \frac{(R_1 + R_4)(R_2 R_5) + (R_2 + R_5)(R_1 R_4)}{R_1 R_4 R_2 R_5}$$

B No, the Thevenin voltage V_{th} in part A and the bridge voltage aren't equal. This is a result of the serial capacitors which does not let us directly determine the results of the bridge, so it is not possible to determine if the resistors and voltages are equal.

$$D \quad I = \frac{V}{R} = \frac{(V_1 - V_{th})(R_1)(R_2 + R_5) + (R_5)(R_1 + R_4)}{(R_1 + R_4)(R_2 + R_5)}$$

$$2 \frac{(R_1 + R_4)(R_2 R_5) + (R_2 + R_5)(R_1 R_4)}{R_1 R_4 R_2 R_5}$$

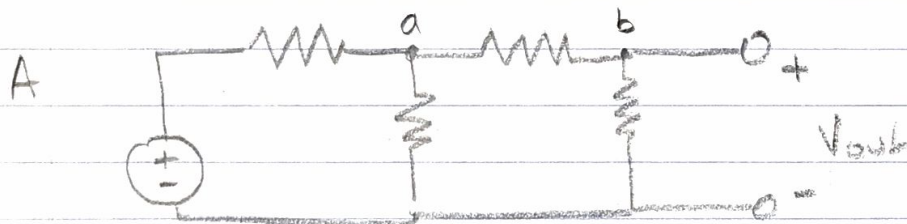4 DAC $V_{out} = V_s \sum_{n=0}^N \frac{1}{2^n} \cdot b_n$




At point A $V = V_{R_{son}} = \frac{1}{2} V_s$ (parallel resistors)

Voltage = $\frac{1}{2} V_s$ correspondingly as if remaining constant

Yes $V_{out} = \frac{1}{4} V_s$ (Parallel Resistors)


B

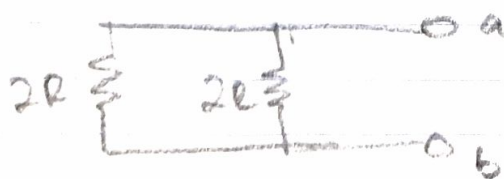

$$R_{eq} = \frac{1}{2} 2R = R$$


(Parallel Resistors)
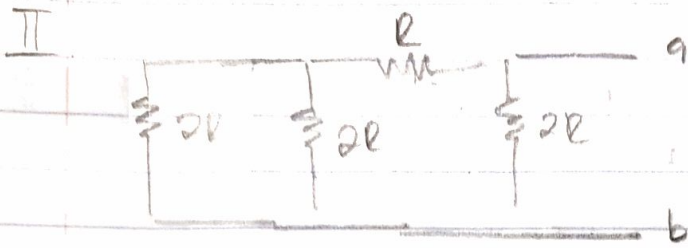
$$\frac{1}{2R} + \frac{1}{2R} = \frac{2}{2R} = R \checkmark$$




$$R_{eq} = \frac{1}{2R} + \frac{1}{R} + \frac{1}{2R} + \frac{1}{2R}$$
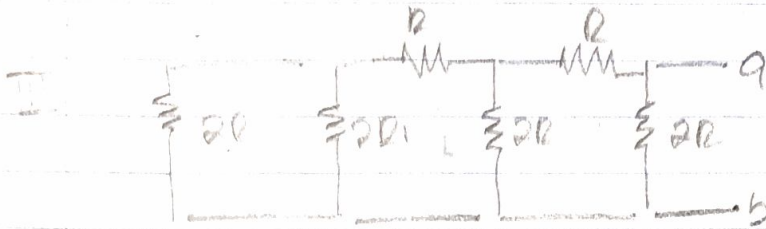
$$R_{eq} = \frac{1 + 2 + 1 + 1}{2R} = \frac{2R}{5}$$



$$R_{eq} = 2 \cdot \frac{1}{R} + 4 \cdot \frac{1}{2R} =$$
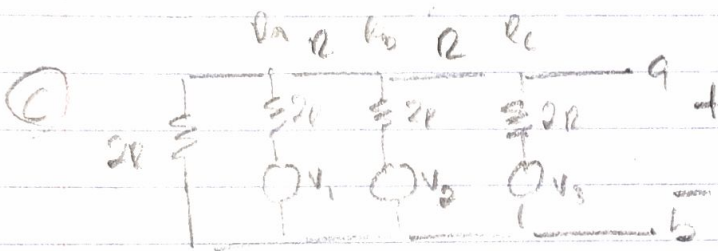
$$\frac{4}{2R} + \frac{4}{2R} = \frac{8}{2R} = \frac{4}{R}$$



$$V_{out} = V_1 \cdot \frac{1}{2} (2R) + V_2 \left(\frac{1}{2} \left(\frac{1}{2R} + \frac{1}{R} + \frac{1}{2R} \right) \right)$$

$$= V_1 R + V_2 \left(\frac{2+2+1}{2R} \right) = \left(\frac{5}{2R} \right) = \frac{5}{2} R$$

$$= V_1 R + V_2 \frac{1}{2R} + V_3 \left(\frac{1}{2} \left(\frac{1}{2R} + \frac{1}{R} + \frac{1}{2R} \right) \right)$$


$$= V_1 R + V_2 \frac{1}{2} R + V_3 \frac{1}{2} \left(\frac{2}{10R} + \frac{10}{10R} + \frac{5}{10R} \right) =$$

$$V_1 R + V_2 \frac{1}{2} R + V_3 \frac{1}{2} \frac{10R}{17} = \frac{5}{17} R$$

$$= V_1 R + V_2 \frac{1}{2} R + V_3 \frac{5}{17} R$$

IV
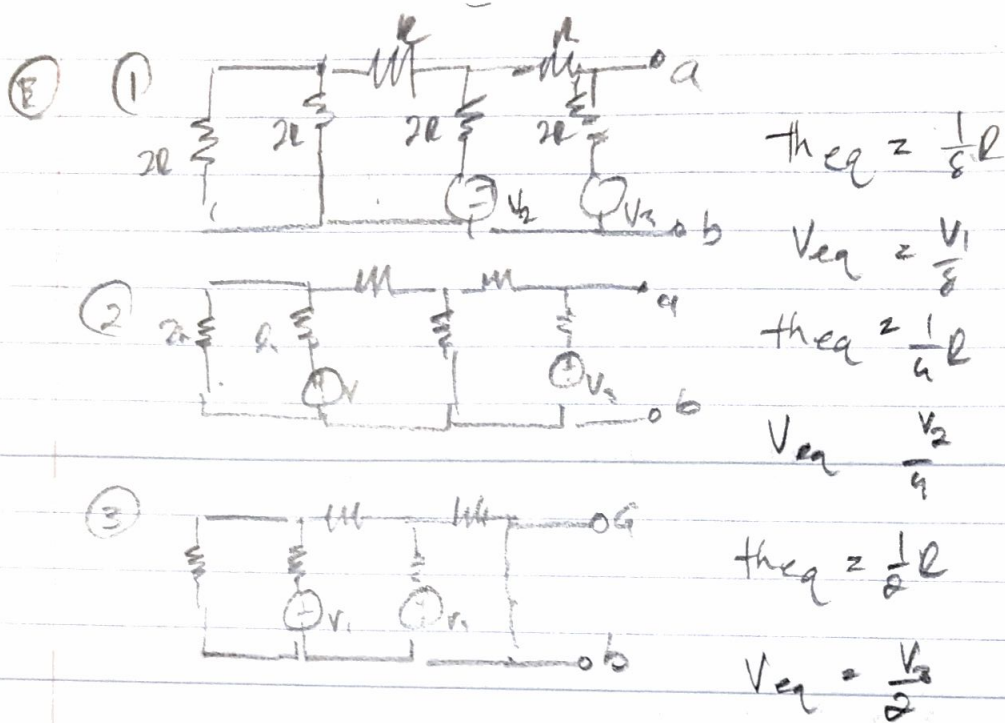
$$V_{out} = \boxed{\frac{1}{5} \text{ Volts}}$$



④ The voltage across the speaker, is less because the speaker acting like a resistor, drops the voltage. This is essentially adding another resistor, but it is not in parallel so it does not lower the resistance, it increases the resistance, overall lowering the voltage of the system so it is less than what we computed in part D.

⑤ Maximum horsepower. $V = IR$ $P = V \cdot I$

A The power delivered by the voltage source is

$R_{eq} = R_s$ (series resistors) $\frac{P}{V} = I$

$V_{out} = V_s \cdot (R_s + R_{motor}) I$ $V = \frac{P}{I}$ $P = \frac{V^2}{R}$

$P = \frac{V_s^2}{(R_s)^2}$ power delivered to resistor (R_{motor})

5

B $P_{\text{motor}} = 1 \cdot V$

$$V = IR \quad I = \frac{V}{R}$$

$$P_{\text{motor}} = \frac{V^2}{R} \quad \text{where } R_{\text{eq}} = R_s + R_{\text{motor}}$$

$$= \frac{V_s^2}{(R_s + R_{\text{motor}})}$$




C $\frac{dP}{dR} = \frac{-V^2}{R^2} = \frac{-V_s^2}{(R_s + R_{\text{motor}})^2} = 0 \text{ when } -V_s^2 = 0$

D $P = \frac{V^2}{R} \rightarrow \frac{V_s^2}{R_s}$ (in order to maximize power to the motor, we need to minimize the resistance at R_s . As $R_s \downarrow$, $P \uparrow$ so they have an inverse relationship

(as close to zero but not zero)

6 Super Capacitor

A

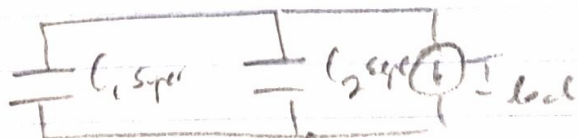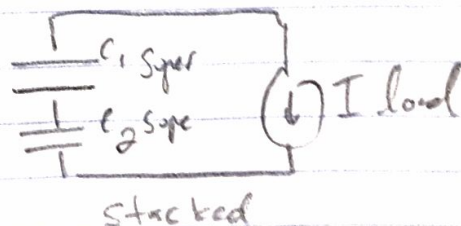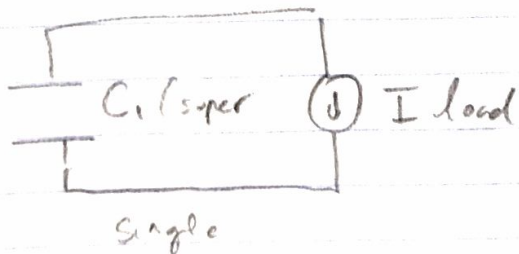

B I $Q_{sc} = C_{sc} V_s \rightarrow V_s = \frac{Q_{sc}}{C_{sc}}$

$$\frac{dV}{dt} = \frac{1}{C_{sc}} \cdot \frac{dQ_{sc}}{dt} = -\frac{I_{load}}{C_{sc}}$$

$$dV = -\frac{I_{load}}{C_{sc}} dt$$

$$V = \int_{t_0}^t dV = \int_{t_0}^t -\frac{I_{load}}{C_{sc}} dt = -\frac{I_{load} t}{C_{sc}} +$$

$$= \left[-\frac{I_{load} t}{C_{sc}} - \frac{I_{load} t_0}{C_{sc}} + V(t_0) \right]$$

I $C_{eq} = \frac{C_{sc}^2}{2C_{sc}} \quad Q_{sc} = C_{eq} V_s$

$$V = \frac{Q_{sc}}{C_{eq}} \rightarrow \frac{dV}{dt} = -\frac{I_{load}}{C_{eq}} \rightarrow dV = -\frac{I_{load}}{C_{eq}} dt$$

$$V(t) = \int dV + V(0) = -\frac{I_{load}}{C_{eq}} dt + V(0)$$

$$V_2(t) = \left[-\frac{2 C_{eq} I_{load} t}{C_{eq}^2} + V(0) \right]$$

$$V(0) = V_{int}$$

II $C_{eq} = 2C_{sc}$

$$V_3(t) = \left[\frac{I_{load} t}{2C_{sc}} + V(0) \right]$$




C I $V_1(t) = V_{\text{max}} - \frac{I_{\text{load}} t}{C_{\text{sc}}} \rightarrow V_{\text{min}} \rightarrow V_{\text{max}} - V_{\text{min}} =$
 $\frac{I_{\text{load}} t}{C_{\text{sc}}} \rightarrow \frac{C_{\text{sc}} (V_{\text{max}} - V_{\text{min}})}{I_{\text{load}}}$

II $V_0(t) = V = \frac{C_{\text{sc}} (V_{\text{max}} - V_{\text{min}})}{2 I_{\text{load}}}$

III $V_{\text{avg}} \rightarrow \frac{2 C_{\text{sc}} (V_{\text{max}} - V_{\text{min}})}{I_{\text{load}}}$

D 2 super capacitors stacked in parallel has a longer life and is more efficient.

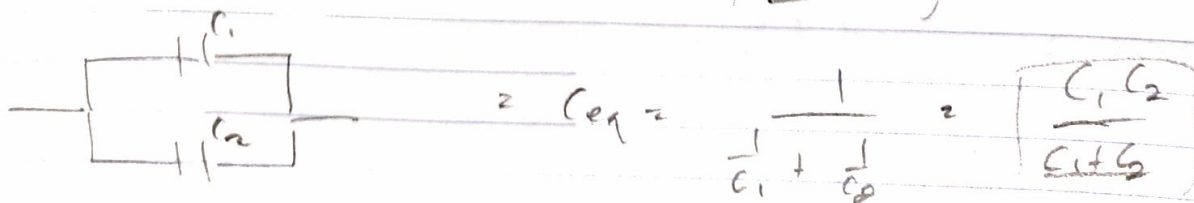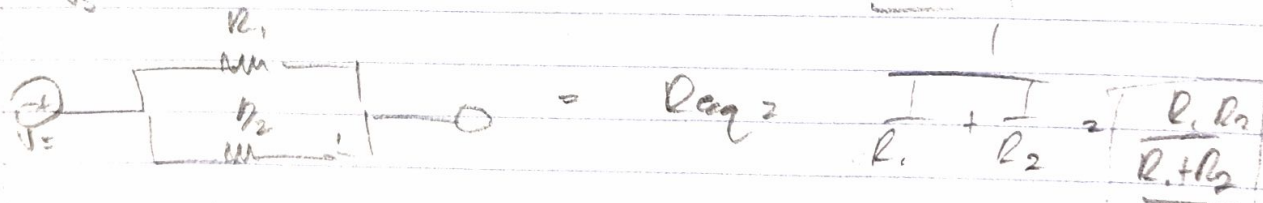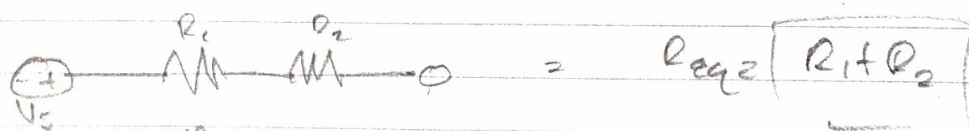7 Write all the basic way for series and parallel resistors and capacitors and calculate the equivalent resistors & capacitance.



P6 8

8. I worked on this homework assignment alone.