


## EEKA HW 7

- ①  $M_1 \rightarrow$  resistivity  $\rho$   
 $M_2 \rightarrow$  resistivity  $\rho$

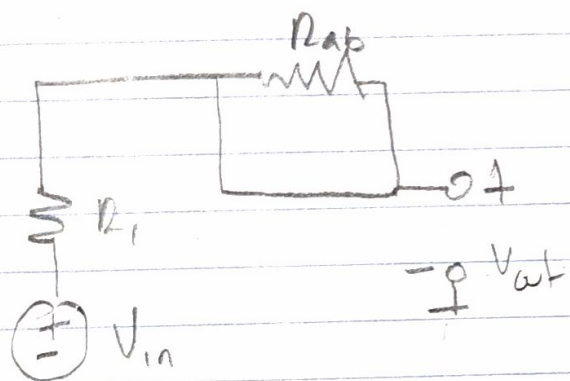A.  $R_{AB} =$  resistivity of  $M_1$  + resistivity of  $M_2$

The length of each bar is  $L + \frac{1}{2}L$

$$R_{AB} = R_1 + R_2 = \left[ \rho \frac{(L + \frac{1}{2}L) \times 2}{A} \right]$$



$$V_{out} = -\frac{R_{AB}}{R_1} V_{in}$$

2770 mAh at 3.8 V = 10526 mWhr  
 0.4 W  $\rightarrow$  400 mW  $\frac{10,526 \text{ mWhr}}{400 \text{ mW}} = 26.315 \text{ Hrs.}$

1 Joule = 1 W second

$\frac{10,526 \text{ mWhr}}{1 \text{ W second}} \times \frac{1 \text{ W}}{1000 \text{ mW}} \cdot \frac{3600 \text{ sec}}{1 \text{ hr}} = 37,8936 \text{ KJ}$

1 Amp = 1 Coulomb/sec  $2770 \text{ mA hr} \times \frac{3600 \text{ sec}}{1 \text{ hr}}$

= 9972000 mAs = 9972000 Coulombs  
 $9972000 \cdot 1.602 \times 10^{-19} = 6.224719 \times 10^{15} \text{ Electrons.}$

From previous question 2770 mAh @ 3.8 V = 10526 mWhr

10,526 mWhr  $\cdot$  31 Days = 326,306 mWhr over 31 days

$\approx 0.326306 \text{ kWhr} \cdot \frac{12 \text{¢}}{\text{kWh}} = \text{approximately } 4 \text{ cents.}$

Energy = power  $\cdot$  time

$P = I^2 R_{\text{bat}}$  200 m $\Omega$  resist +  $R_{\text{bat}}$  in series  
 $V = IR$   $I = \frac{V}{R}$   $I = \frac{5 \text{ V}}{200 \text{ m}\Omega + R_{\text{bat}}}$

$P = \left( \frac{5}{200 \text{ m}\Omega + R_{\text{bat}}} \right)^2 R_{\text{bat}}$

$\frac{dP}{dR_{\text{bat}}} \left[ \frac{25 R_{\text{bat}}}{(R_{\text{bat}} + \frac{1}{5})^2} \right] = 25 \cdot \frac{d(x) \cdot (x + \frac{1}{5})^2 - x \cdot d(x + \frac{1}{5})^2}{(x + \frac{1}{5})^4}$   
 let  $R_{\text{bat}} = x$

$$(40) = 25 \cdot \frac{1 \cdot (x + \frac{1}{5})^2 - 2x \cdot (x + \frac{1}{5}) \cdot \frac{1}{5} (x + \frac{1}{5})}{(x + \frac{1}{5})^4}$$

$$= 25 \left( (x + \frac{1}{5})^2 - 2(1 + 0)x(x + \frac{1}{5}) \right)$$

$$= 25 \left( (x + \frac{1}{5})^2 - 2x(x + \frac{1}{5}) \right)$$

$$= \frac{25}{(x + \frac{1}{5})^2} - \frac{50x}{(x + \frac{1}{5})^3} = \frac{25(x + \frac{1}{5}) - 50x}{(x + \frac{1}{5})^3}$$

$$= \frac{25x + 5 - 50x}{(x + \frac{1}{5})^3} = \frac{-25x + 5}{(x + \frac{1}{5})^3}$$

$$\frac{-25(x - \frac{1}{5})}{(x + \frac{1}{5})^3} \quad \frac{db}{dR_{bat}} = 0 \text{ when } x = \frac{1}{5} = R_{bat}$$

$$\frac{1}{5} \Omega = 200 \text{ m}\Omega$$

$$R_{\text{Total in series}} = 400 \text{ m}\Omega$$

$$\text{so the battery will be } \frac{5V}{0.4\Omega} = 12.5 \text{ Amps}$$

$$P_{bat} = I_{r_{bat}}^2 \cdot R_{bat} = 12.5^2 \times 0.2 = 31.25 \text{ watts}$$

to get charge time

$$\frac{10.526 \text{ Whr}}{31.25 \text{ watts}} \approx 20 \text{ minutes}$$



Ex 1.5  
Sens.

A  $R_2$  abbrechen, ne em see  $R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$

$$V_{out} = \frac{R_1 R_2 - V_S}{R_1 + R_2}$$

B  $R_2$  abbrechen,  $V_{out} = \frac{R_1 R_2}{R_1 + R_2} V_S \cdot R_0 (1 + \alpha T)$

$$V_{out} = \frac{R_1 R_0 (1 + \alpha T)}{R_1 + (R_0)(1 + \alpha T)} \cdot V_S$$

$$(V_{out})(R_1) + (V_{out})(R_0)(1 + \alpha T) = (R_1 R_0)(1 + \alpha T) V_S$$

$$(V_{out})(R_1) = (R_1 R_0)(1 + \alpha T)(V_S) - (V_{out})(R_0)(1 + \alpha T)$$

$$\frac{(V_{out})(R_1)}{(R_1 R_0)(V_S) - (V_{out})(R_0)} = (1 + \alpha T)$$

$$\frac{(V_{out})(R_1)}{(R_0)(R_1 V_S - V_{out})} - 1 = T$$

Ex

$$i_{sc} = \frac{R_1 R_2}{R_1 + R_2} = \frac{R_1 (1 + \beta T) R_2 (1 + \alpha T)}{(R_1 (1 + \beta T) + R_2 (1 + \alpha T))}$$

$$i_{sc} (R_1 (1 + \beta T) + R_2 (1 + \alpha T)) = R_1 (1 + \beta T) R_2 (1 + \alpha T)$$

$$i_{sc} (R_1 - \beta T + R_2 + \alpha T) = 1 + \beta T + \alpha T + \beta \alpha T^2$$

$$i_{sc} \left( \frac{R_1 + R_2 + R_2 \alpha T}{R_1 R_2} \right) - 1 = T (\beta + \alpha + \beta \alpha T)$$

$$\frac{i_{sc}}{R_2} + \frac{i_{sc} \beta T}{R_2} - \frac{V_{oc}}{R_1} + \frac{V_{oc} \alpha T}{R_1} - 1 = (-\beta T) (1 + \alpha T)$$

$$i_{sc} \left( \frac{1}{R_2} + \frac{1}{R_1} \right) = \frac{(1 + \beta T) (1 + \alpha T) - V_{oc} \beta T - V_{oc} \alpha T}{R_2 R_1}$$

Ex  $V_{oc} = \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{R_1 R_2 (1 + \alpha T)}{R_1 (1 + \beta T) + R_2 (1 + \alpha T)} = \frac{R_1 R_2}{R_1 + R_2} (1 + \alpha T)$

$$\frac{i_{sc}}{V_{oc}} \cdot \frac{R_1 + R_2}{R_1 R_2} = 1 + \alpha T$$

$$\frac{V_{oc}}{V_{is}} \cdot \frac{R_1 + R_2}{R_1 R_2} - 1 = T$$


yes, this circuit can be used to measure temperature

Problem 6A  
Resistor  
Temperature

$$R = \rho \cdot \frac{L}{A} \Rightarrow R_{E_1-E_2} = \rho \left( \frac{L}{W \cdot t} \right)$$

$$R_{E_1-E_2} = 1 \Omega \cdot \left( \frac{12 \times 10^{-2} \text{ m}}{3 \times 10^{-2} \cdot 0.5 \times 10^{-3} \text{ m}} \right)$$

$$R_{E_1-E_2} = 8 \text{ k}\Omega$$

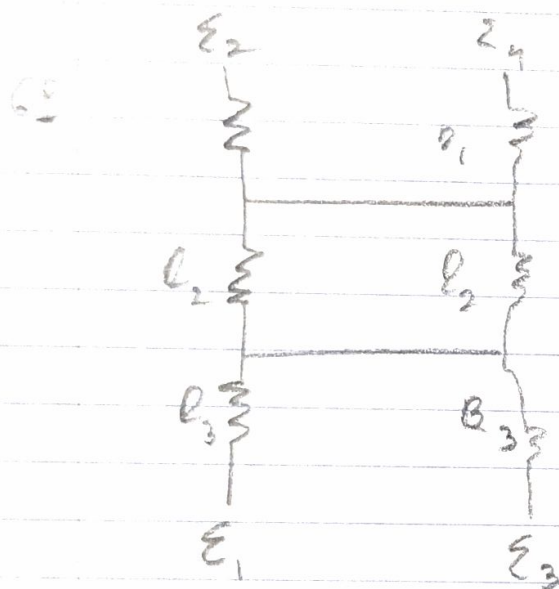

$$R_2 = \frac{3 \text{ cm}}{12 \text{ cm}} \cdot R_{E_1-E_2} = 1.25 \text{ k}\Omega$$

$$R_2 = \frac{7-3 \text{ cm}}{12 \text{ cm}} \cdot R_{E_2-E_1} = 1.667 \text{ k}\Omega$$

$$R_1 = \frac{12-7 \text{ cm}}{12 \text{ cm}} \cdot R_{E_2-E_1} = 2.0833 \text{ k}\Omega$$

6C. Equivalent resistance between  $E_4 - E_3$  is


$$R_{E_4-E_3} = R_1 + R_2 \parallel R_2 + R_3 = R_1 + \frac{R_2}{2} + R_3$$

$$= 1.25 \text{ k}\Omega + \frac{1.667 \text{ k}\Omega}{2} + 2.0833 \text{ k}\Omega$$

$$\approx 4.67 \text{ k}\Omega$$

$$V_{E_4-E_3} = 1 \text{ mA} \cdot R_{E_4-E_3} \Rightarrow V_{E_4-E_3} = 4.67 \text{ V}$$

60

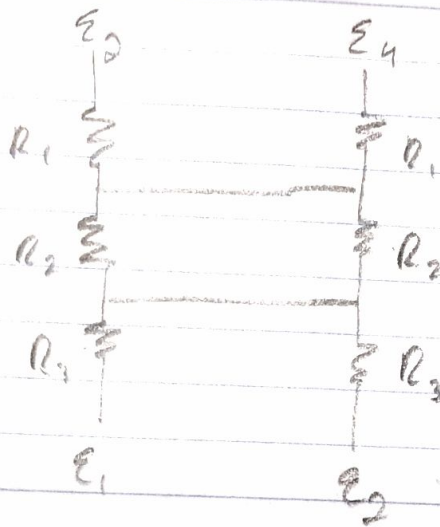

$$R_{22} = \frac{g_1}{12\text{cm}} \cdot 5\text{k}\Omega$$

$$R_{22} = \frac{g_2 - g_1}{12\text{cm}} \cdot 5\text{k}\Omega$$


$$R_{12} = \frac{12\text{cm} - g_2}{12} \cdot 5\text{k}\Omega$$

$$R_{eq} = R_3 + R_1 + \frac{R_2}{2} + R_3 = \left( 12\text{cm} - g_2 + \frac{g_2 - g_1}{2} + g_1 \right) \cdot \frac{5\text{k}\Omega}{12\text{cm}}$$

$$= \left( 12\text{cm} + \frac{g_1}{2} - \frac{g_2}{2} \right) \cdot \frac{5\text{k}\Omega}{12\text{cm}}$$

$$V_{eq} = E_1 = \frac{12\text{cm} (g_2 - g_1)}{12} \cdot 5\text{V}$$

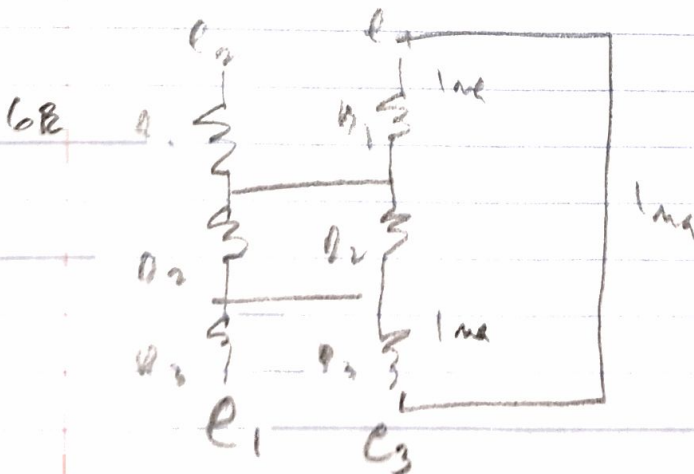We can send across the divider between the two touch points



$$V_{E1-E2} = I_{R1} = \frac{12\text{cm} - g_2}{12\text{cm}} \cdot 5\text{V}$$

$$V_{E1-E3} = I_{R3} = \frac{g_1}{12\text{cm}} \cdot 5\text{V}$$



7 Find the mWh of the Samsung Galaxy S8t with 3500mAh battery @ 3.85V

A  $3500 \cdot 3.85 = 13475 \text{ mWh}$

B Convert to joules  $13475 \times 3.6 \frac{\text{sec}}{\text{hr}} = 348510$

C Convert to calms  $3500\text{mAh} \times \frac{3600\text{sec}}{\text{hr}} = 12600000 \text{ Calms}$

8 I worked on this assignment alone.